

Electric Circuits



MODULE 3



What's inside those wires?




Concept	Symbol	Unit	Definition
Current	<i>i</i>	Amps (A)	The measure of electron flow in a circuit
Voltage	V	Volts (V)	Difference in electrical potential used to drive electrons around a circuit
Resistance	R	Ohms (Ω)	The measure of how difficult it is for electrons to flow through a circuit

Ohm's Law

$$V = i \times R$$

This formula relates these three important electrical quantities.



Ohm's Triangle

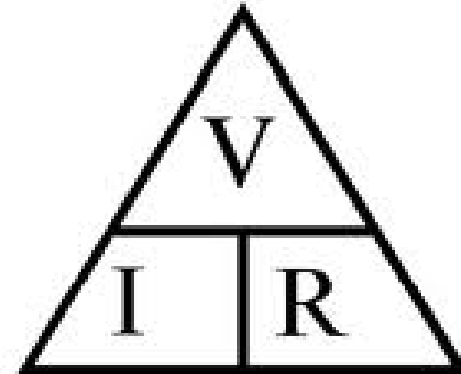

Cover the variable you want to find and perform the resulting calculation (*Multiplication/Division*) as indicated.

Making electrons flow

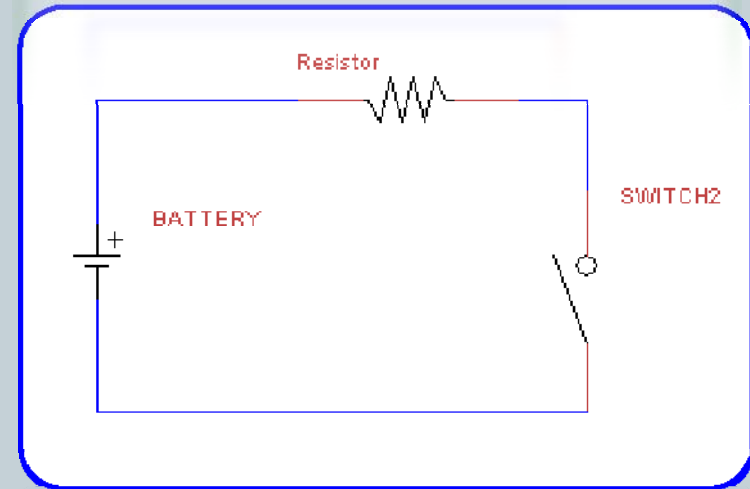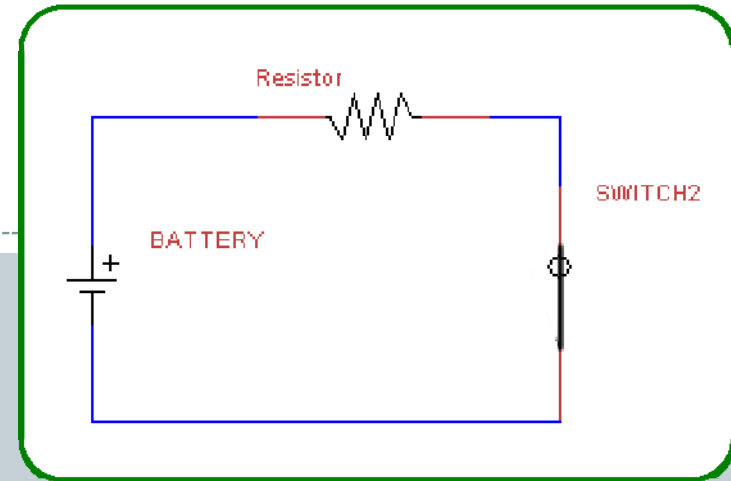 

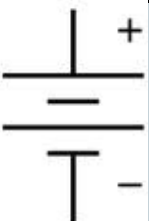
- **Current only flows if it has a continuous path to a lower voltage.**
 - The top picture shows a closed path (current will flow).
 - The bottom picture shows an open path (current will not flow).



Learning to read circuits

- Symbols are used to represent different components in a circuit. Once you recognize the symbols you can read the circuit.




Wire		Wires connect the other components and create continuous path for the current.
Resistor		Resistors have a fixed resistance and can change the value of the current according to Ohm's Law.
Battery		Supplies a portable power supply.

More Symbols




Button

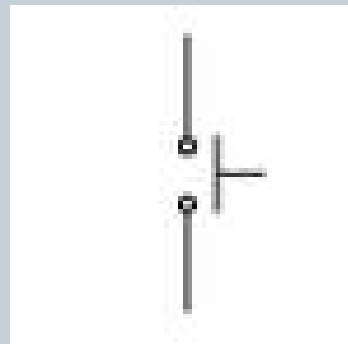

Buttons are used to either (a) open/close a circuit to flow or (b) switch between two different circuits. Note that there is a normal position (either up or down) that the button will return to with no user input.



Switch

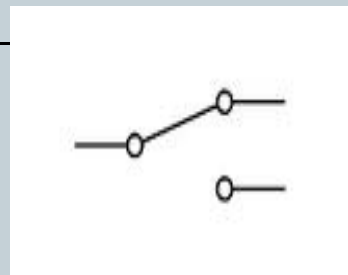


Similar to a button, but there is no normal state, the switch stays where the user puts it.

Different Paths to Follow

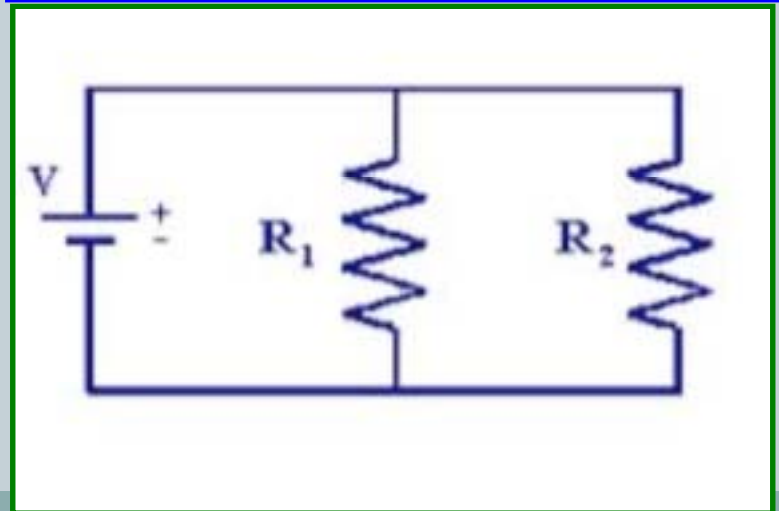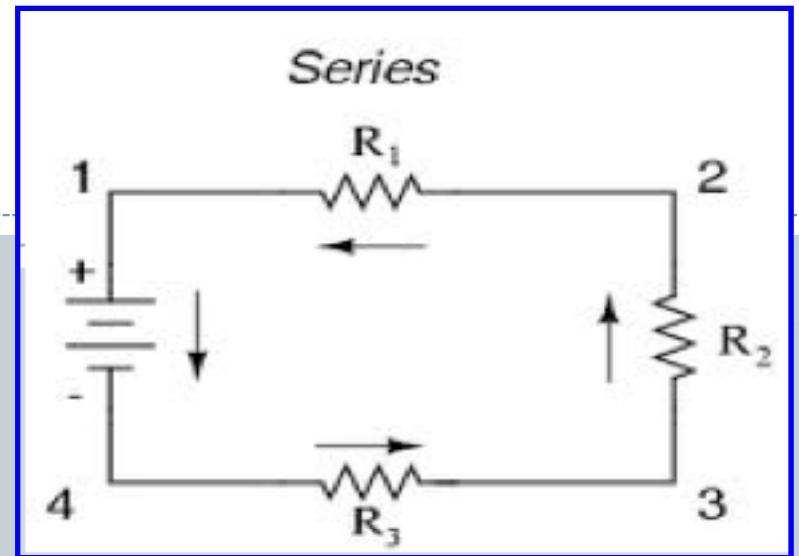
- Series circuits have a single path the current can follow. The current is the same everywhere in the circuit.
- Parallel circuits have more than one path so the current splits apart to pass through the different paths.



What does this circuit represent?

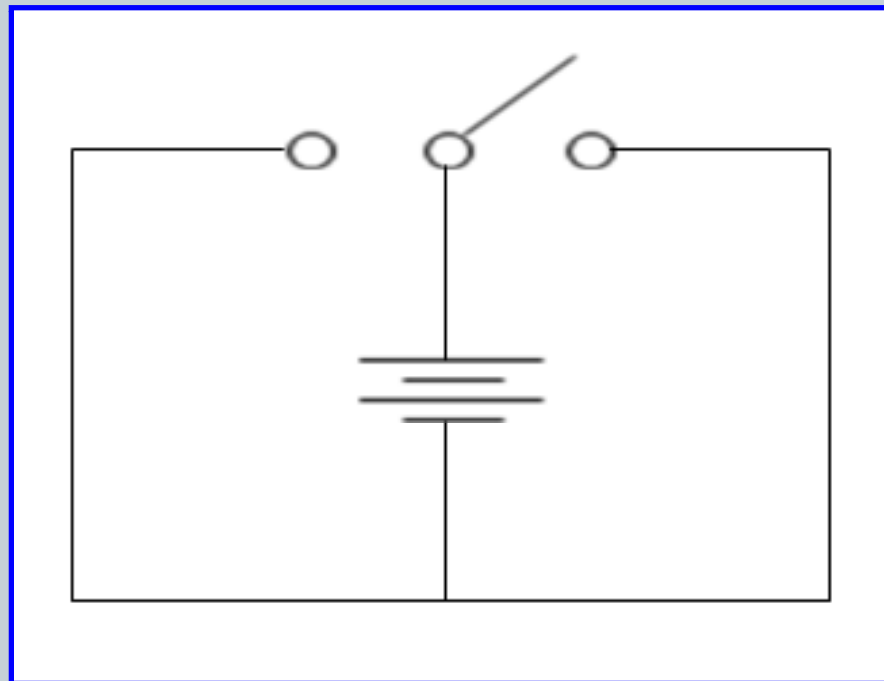

Motors in a circuit

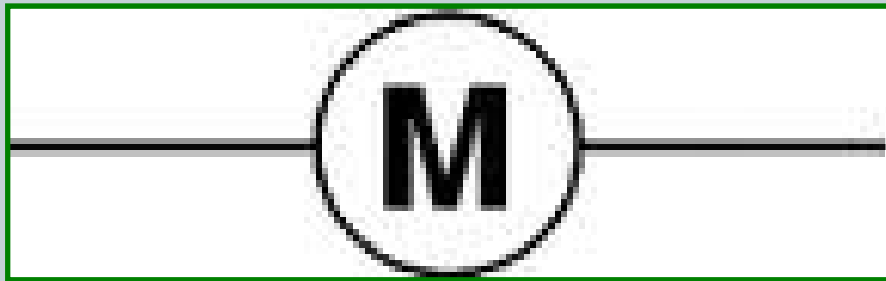

- **What determines the direction the motor spins?**
 - Spin depends on the direction of the current
 - Spin also depends on how the battery terminals are connected

Motor Speed



- **Related to current applied to the motor**
 - **More Current = More Force = Faster Speed**
 - **How do you vary the current?**
 - ✦ **Ohm's law relationship between voltage, current and resistance**
 - ✦ **Use variable voltage source**
 - ✦ **Change resistance of motor**

Circuits in the Sea Perch



- **Can you design, test, and build circuits to control the speed and direction of each of your motors?**
- **Brainstorm with your group and draw circuit diagrams to represent your ideas.**